


Unit 5: Electricity and Magnetism

Review of Electrostatics:

1. Law of Electric Charges

- like charges repel
- unlike charges attract
- neutral → both




2. Conductors vs Insulators and more


Conductor
Insulator
resistor
semiconductor
Superconductor

3. Methods of charging an object

contact
neg



+ by induction



Electric Force (Coulomb's Law)

$$F_{el} = k \frac{Q_1 Q_2}{r^2}$$

$$k = 9 \times 10^9 \frac{Nm^2}{C^2}$$

arbitrary

$$G = 6.67 \times 10^{-11}$$

$$e = 1.6 \times 10^{-19} C$$


charge on 1 electron

-e Q = ne

Series vs Parallel

Series


- one path

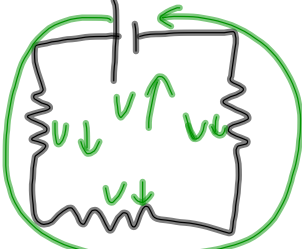

- current is constant everywhere
- voltage is split (not always equally)

Parallel

- several paths

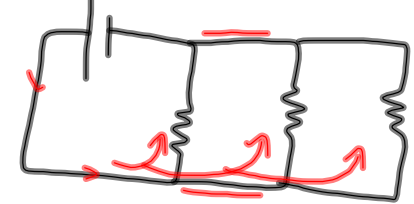


- current splits (not always equally)
- voltage is the same in "each branch"

What about combination circuits?

Kirchhoff's Laws

- Kirchhoff's Current Law (KCL)**
 - the current entering a junction is the same as the current leaving it
- Kirchhoff's Voltage Law (KVL)**
 - in any "loop" of a circuit, the voltage gained must be equal to the voltage lost



	5	1	2	3	4	5
V	12V	8V	4V	4V	3V	1V
I	1A	1A	0.2A	0.4A	0.4A	0.4A


$V_5 = V_1 + V_2$
 $V_5 = V_1 + V_3$

$\therefore V_2 = V_3$

$I_5 = I_1$

$I_5 = I_2 + I_3$

Equivalent Resistance

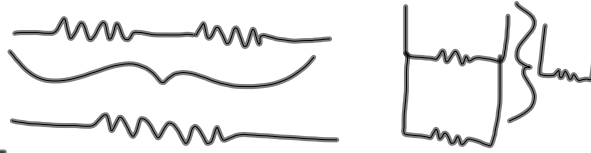

In series...



$$R_s = \frac{V_s}{I_s} \quad \left\{ \begin{array}{l} \text{but in series} \\ V_s = V_1 + V_2 + V_3 + \dots \end{array} \right.$$

$$= \frac{V_1 + V_2 + V_3 + \dots}{I_s}$$

$$= \frac{V_1}{I_s} + \frac{V_2}{I_s} + \frac{V_3}{I_s} + \dots \quad \text{but } I_s = I_1 = I_2 = \dots$$

$$= \frac{V_1}{I_1} + \frac{V_2}{I_2} + \frac{V_3}{I_3} + \dots$$

$$R_s = R_1 + R_2 + R_3 + \dots$$

In parallel...

$$R_p = \frac{V_p}{I_p}$$

$$\frac{1}{R_p} = \frac{I_p}{V_p}$$

$$\text{but } I_p = I_1 + I_2 + I_3 + \dots *$$

$$\therefore \frac{1}{R_p} = \frac{I_1 + I_2 + I_3 + \dots}{V_p}$$

$$\text{but } V_p = V_1 = V_2 = V_3 + \dots *$$

$$\frac{1}{R_p} = \frac{I_1}{V_p} + \frac{I_2}{V_p} + \frac{I_3}{V_p} + \dots$$

$$= \frac{I_1}{V_1} + \frac{I_2}{V_2} + \frac{I_3}{V_3} + \dots$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

What is the total resistance when a 100Ω, 50Ω and 30Ω resistor are added in parallel?

$$\frac{1}{R_p} = \frac{1}{100} + \frac{1}{50} + \frac{1}{30}$$

$$= \frac{3}{300} + \frac{6}{300} + \frac{10}{300}$$

$$\frac{1}{R_p} = \frac{19}{300}$$

$$R_p = \frac{300}{19}$$


$$= 15.8\Omega$$

Combination Circuits

What is R_T ?

$$R_{34} = R_3 + R_4$$

$$= 30 + 40$$

$$= 70 \Omega$$


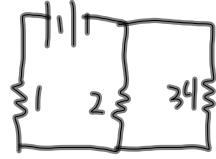
$$R_T = R_1 + R_{234}$$

$$= 10 + 15.6$$

$$R_T = 25.6 \Omega$$

$R_4 = 40 \Omega$

$R_3 = 30 \Omega$




$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_{34}}$$

$$= \frac{1}{20} + \frac{1}{70}$$

$$= \frac{7+2}{140}$$

$$= \frac{9}{140}$$
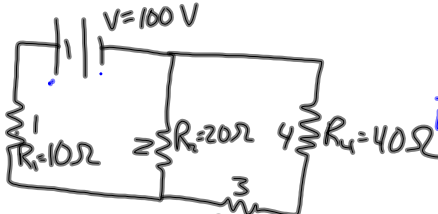
$$R_{234} = \frac{140}{9} = 15.6 \Omega$$



$\frac{1}{R} = 25$

V(V)	T	1	2,3,4	3	4
100	39.1	60.9	25.8	34.4	
I(A)	3.91	3.91	3.05	0.86	0.86
R(Ω)	25.6	10	20	30	40

$V_3 + V_4 = 25.8 + 34.4 = 60.2$

- ① $R = \frac{V}{I} \therefore I_T = \frac{V_T}{R_T} = \frac{100}{25.6} = 3.91$
- ② $I_T = I_1$ (KCL)
- ③ $V = IR = 3.91 \times 10 = 39.1 V$
- ④ $V_T = V_1 + V_2$ (KVL)
 $V_2 = V_T - V_1 = 60.9 V$
- ⑤ $I_2 = \frac{V_2}{R_2} = \frac{60.9}{20} = 3.05$
- ⑥ $I_T = I_2 + I_3$
 $\therefore I_4 = 3.91 - 3.05 = 0.86 A$
- ⑦ $V_3 = I_3 R_3 = (0.86)(30) = 25.8 V$
- ⑧ $V_4 = 34.4 V$

Power & Electrical Cost

We know $P = \frac{\Delta E}{t}$

but $V = \frac{\Delta E}{Q}$ so $\Delta E = VQ$

$$\therefore P = \frac{VQ}{t} = V\left(\frac{Q}{t}\right) = VI$$

$$P = VI$$

Eg. $P = 32 \text{ W}$
 $V = 120 \text{ V}$
 $I = ?$

$$P = VI$$

$$I = \frac{P}{V}$$

$$= \frac{32}{120}$$

$$= 0.27 \text{ A}$$

Cost of Electricity

We pay for the energy we use.

Different units can be used...

$$P \Rightarrow \text{kW}$$

$$t \Rightarrow \text{h}$$

$$E = Pt$$

\downarrow \downarrow \downarrow
 kWh kWh h
 ↳ kilowatt hours

1 kWh is the energy used by a 1000 W device in 1 h.

rate $6 \frac{\$}{\text{kWh}} \rightarrow 12 \frac{\$}{\text{kWh}}$

Eg. \rightarrow 100 W bulb
 \rightarrow on 24 h/day for 30 days

$$P = 100 \text{ W}$$

$$= 0.1 \text{ kW}$$

$$t = 24 \times 30$$

$$= 720 \text{ h}$$

$$\text{rate} \sim 8 \frac{\$}{\text{kWh}}$$

$$E = Pt$$

$$= (0.1)(72)$$

$$= 72 \text{ kWh}$$

$$\text{cost} = E \times \text{rate}$$

$$= (72)(0.08)$$

$$= \$5.76$$

$$C = Pt(\text{rate})$$